

Chapter 27. Current and Resistance

Electric Current and Ohm's Law

27-1. How many electrons pass a point every second in a wire carrying a current of 20 A?

How much time is needed to transport 40 C of charge past this point?

$$Q = It = (20 \text{ C/s})(1 \text{ s}); \quad Q = 20 \frac{\text{C}}{\text{s}} \left(\frac{1 e}{1.6 \times 10^{-19} \text{ C}} \right); \quad \boxed{Q = 1.25 \times 10^{20} \text{ electrons/s}}$$

$$I = \frac{Q}{t}; \quad t = \frac{Q}{I} = \frac{40 \text{ C}}{20 \text{ A}} = 2.00 \text{ s}; \quad \boxed{t = 2.00 \text{ s}}$$

27-2. If 600 C of charge pass a given point in 3 s, what is the electric current in amperes?

$$I = \frac{Q}{t} = \frac{600 \text{ C}}{3 \text{ s}}; \quad \boxed{I = 20 \text{ A}}$$

27-3. Find the current in amperes when 690 C of charge pass a given point in 2 min.

$$I = \frac{Q}{t} = \frac{690 \text{ C}}{120 \text{ s}}; \quad \boxed{I = 5.75 \text{ A}}$$

27-4. If a current of 24 A exists for 50 s, how many coulombs of charge have passed through the wire?

$$Q = It = (24 \text{ A})(50 \text{ s}); \quad \boxed{Q = 1200 \text{ C}}$$

27-5. What is the potential drop across a 4- Ω resistor with a current of 8 A passing through it?

$$V = IR = (8 \text{ A})(4 \Omega); \quad \boxed{V = 32.0 \text{ V}}$$

27-6. Find the resistance of a rheostat if the drop in potential is 48 V and the current is 4 A.

$$R = \frac{V}{I} = \frac{48 \text{ V}}{4 \text{ A}}; \quad \boxed{R = 12.0 \Omega}$$

27-7. Determine the current through a 5- Ω resistor that has a 40-V drop in potential across it?

$$I = \frac{V}{R} = \frac{40 \text{ V}}{5 \Omega}; \quad \boxed{I = 8.00 \text{ A}}$$

27-8. A 2-A fuse is placed in a circuit with a battery having a terminal voltage of 12 V. What is the minimum resistance for a circuit containing this fuse?

$$R = \frac{V}{I} = \frac{12 \text{ V}}{2 \text{ A}}; \quad \boxed{R = 6.00 \Omega}$$

7-9. What emf is required to pass 60 mA through a resistance of 20 k Ω ? If this same emf is applied to a resistance of 300 Ω , what will be the new current?

$$E = IR = 60 \times 10^{-3} \text{ A}(20 \times 10^3 \Omega); \quad E = 1200 \text{ V}$$

$$I = \frac{E}{R} = \frac{1200 \text{ V}}{300 \Omega}; \quad \boxed{I = 4.00 \text{ A}}$$

Electric Power and Heat Loss

27-10. A soldering iron draws 0.75 A at 120 V. How much energy will it use in 15 min?

$$P = IV = (0.75 \text{ A})(120 \text{ V}); \quad P = 90.0 \text{ W}; \quad t = 15 \text{ min} = 900 \text{ s}$$

$$P = \frac{\text{Work}}{t}; \quad \text{Energy} = Pt = (90 \text{ W})(900 \text{ s}); \quad \boxed{E = 81,000 \text{ J}}$$

27-11. An electric lamp has an 80- Ω filament connected to a 110-V direct-current line. What is the current through the filament? What is the power loss in watts?

$$I = \frac{V}{R} = \frac{110 \text{ V}}{80 \Omega}; \quad \boxed{I = 1.38 \text{ A}}$$

$$P = \frac{V^2}{R} = \frac{(110 \text{ V})^2}{80 \Omega}; \quad \boxed{P = 151 \text{ W}}$$

27-12. Assume that the cost of energy in a home is 8 cents per kilowatt-hour. A family goes on a 2-week vacation leaving a single 80-W light bulb burning. What is the cost?

$$E = Pt = (80 \text{ W})(2 \text{ wk})(7 \text{ day/wk})(24 \text{ h/day})(3600 \text{ s/h}) = 26.9 \text{ kW h}$$

$$E = (26.9 \text{ kW h})(0.08 \text{ c/kw h}) = \boxed{\$2.15} \quad (\text{Rates vary})$$

27-13. A 120-V, direct-current generator delivers 2.4 kW to an electric furnace. What current is supplied? What is the resistance?

$$I = \frac{P}{V} = \frac{2400 \text{ W}}{120 \text{ V}}; \quad \boxed{I = 20 \text{ A}}; \quad R = \frac{V}{I} = \frac{120 \text{ V}}{20 \text{ A}}; \quad \boxed{R = 6.00 \Omega}$$

27-14. A resistor develops heat at the rate of 250 W when the potential difference across its ends is 120 V. What is its resistance?

$$P = \frac{V^2}{R}; \quad R = \frac{V^2}{P} = \frac{(120 \text{ V})^2}{250 \text{ W}}; \quad \boxed{R = 57.6 \Omega}$$

27-15. A 120-V motor draws a current of 4.0 A. How many joules of electrical energy is used in one hour? How many kilowatt-hours?

$$P = VI = (120 \text{ V})(4.0 \text{ A}) = 480 \text{ W}$$

$$P = \frac{E}{t}; \quad E = Pt = (480 \text{ W})(3600 \text{ s}); \quad \boxed{E = 1.73 \text{ MJ}}$$

$$E = 1.73 \times 10^6 \text{ J} \left(\frac{1 \text{ kW} \cdot \text{h}}{3.60 \times 10^6 \text{ J}} \right) \quad \boxed{E = 0.480 \text{ kW h}}$$

27-16. A household hair dryer is rated at 2000 W and is designed to operate on a 120-V outlet. What is the resistance of the device?

$$P = \frac{V^2}{R}; \quad R = \frac{V^2}{P} = \frac{(120 \text{ V})^2}{2000 \text{ W}}; \quad \boxed{R = 7.20 \Omega}$$

Resistivity

27-17. What length of copper wire 1/16 in. in diameter is required to construct a 20- Ω resistor at 20⁰C? What length of nichrome wire is needed?

$$\text{Copper: } \rho = 1.78 \times 10^{-8} \Omega \cdot \text{m}; \quad \text{nichrome: } \rho = 100 \times 10^{-8} \Omega \cdot \text{m}$$

$$\frac{1}{16} \text{ ft} = 0.0625 \text{ in.} = 62.5 \text{ mil}; \quad A = (62.5 \text{ mil})^2 = 3906 \text{ cmil}$$

$$R = \frac{\rho l}{A}; \quad l = \frac{RA}{\rho} = \frac{(20 \Omega)(3906 \text{ cmil})}{10.4 \Omega \cdot \text{cmil/ft}}; \quad \boxed{l = 7510 \text{ ft}}$$

$$R = \frac{\rho l}{A}; \quad l = \frac{RA}{\rho} = \frac{(20 \Omega)(3906 \text{ cmil})}{600 \Omega \cdot \text{cmil/ft}}; \quad \boxed{l = 130 \text{ ft}}$$

27-18. A 3.0-m length of copper wire ($\rho = 1.78 \times 10^{-8} \Omega \cdot \text{m}$) at 20⁰C has a cross section of 4 mm². What is the electrical resistance of this wire? [$A = 4 \text{ mm}^2 = 4 \times 10^{-6} \text{ m}^2$]

$$R = \frac{\rho l}{A} = \frac{(1.78 \times 10^{-8} \Omega \cdot \text{m})(3.0 \text{ m})}{4.00 \times 10^{-6} \text{ m}^2}; \quad \boxed{R = 12.9 \text{ m}\Omega}$$

27-19. Find the resistance of 40 m of tungsten ($\rho = 5.5 \times 10^{-8} \Omega \cdot \text{m}$) wire having a diameter of 0.8 mm at 20⁰C?

$$A = \frac{\pi D^2}{4} = \frac{\pi(0.0008 \text{ m})^2}{4}; \quad A = 5.03 \times 10^{-7} \text{ m}^2$$

$$R = \frac{\rho l}{A} = \frac{(5.5 \times 10^{-8} \Omega \cdot \text{m})(40.0 \text{ m})}{5.03 \times 10^{-7} \text{ m}^2}; \quad \boxed{R = 4.37 \Omega}$$

27-20. A certain wire has a diameter of 3 mm and a length of 150 m. It has a resistance of 3.00 Ω at 20⁰C. What is the resistivity? [$A = \pi D^2/4 = 7.07 \times 10^{-7} \text{ m}^2$.]

$$R = \frac{\rho l}{A}; \quad \rho = \frac{RA}{l} = \frac{(3 \Omega)(7.07 \times 10^{-7} \text{ m}^2)}{150 \text{ m}}; \quad \boxed{\rho = 1.41 \times 10^{-8} \Omega \cdot \text{m}}$$

27-21. What is the resistance of 200 ft of iron ($\rho = 9.5 \times 10^{-8} \Omega \cdot \text{m}$) wire with a diameter of 0.002 in. at 20°C? ($\rho = 9.5 \times 10^{-8} \Omega \cdot \text{m}$). [200 ft = 61.0 m; 0.002 in. = $5.08 \times 10^{-5} \text{ m}$]

$$A = \frac{\pi D^2}{4} = \frac{\pi(5.08 \times 10^{-5} \text{ m})^2}{4}; \quad A = 2.03 \times 10^{-9} \text{ m}^2$$

$$R = \frac{\rho l}{A} = \frac{(9.5 \times 10^{-8} \Omega \cdot \text{m})(61.0 \text{ m})}{5.08 \times 10^{-9} \text{ m}^2}; \quad \boxed{R = 2860 \Omega}$$

*27-22. A nichrome wire ($\rho = 100 \times 10^{-8} \Omega \cdot \text{m}$) has a length of 40 m at 20°C. What is the diameter if the total resistance is 5 Ω ?

$$R = \frac{\rho l}{A}; \quad A = \frac{\rho l}{R} = \frac{(100 \times 10^{-8} \Omega \cdot \text{m})(40 \text{ m})}{5.00 \Omega}; \quad A = 8 \times 10^{-6} \text{ m}^2$$

$$A = \frac{\pi D^2}{4}; \quad D = \sqrt{\frac{4A}{\pi}} = \sqrt{\frac{2(8 \times 10^{-6} \text{ m}^2)}{\pi}}; \quad \boxed{D = 2.26 \text{ mm}}$$

*27-23. A 115-V source of emf is attached to a heating element which is a coil of nichrome wire ($\rho = 100 \times 10^{-8} \Omega \cdot \text{m}$) of cross section 1.20 mm². What must be the length of the wire if the resistive power loss is to be 800 W? [$A = 1.20 \text{ mm}^2 = 1.20 \times 10^{-6} \text{ m}^2$]

$$P = \frac{V^2}{R}; \quad R = \frac{V^2}{P} = \frac{(115 \text{ V})^2}{800 \text{ W}} = 16.5 \Omega; \quad R = 16.5 \Omega$$

$$R = \frac{\rho l}{A}; \quad l = \frac{RA}{\rho} = \frac{(16.5 \Omega)(1.20 \times 10^{-6} \text{ m}^2)}{100 \times 10^{-8} \Omega \cdot \text{m}}; \quad \boxed{l = 19.8 \text{ m}}$$

Temperature Coefficient of Resistance

27-24. The resistance of a length of wire ($\alpha = 0.0065/\text{C}^0$) is 4.00 Ω at 20°C. What is the resistance at 80°C? [$\Delta t = 80^\circ\text{C} - 20^\circ\text{C} = 60 \text{ C}^0$]

$$\Delta R = \alpha R_0 \Delta t = (0.0065/\text{C}^0)(4 \Omega)(60 \text{ C}^0) = 1.56 \Omega; \quad R = 4.00 \Omega + 1.56 \Omega = \boxed{5.56 \Omega}$$

27-25. If the resistance of a conductor is 100Ω at 20°C , and 116Ω at 60°C , what is its temperature coefficient of resistivity? [$\Delta t = 60^\circ\text{C} - 20^\circ\text{C} = 40 \text{ C}^\circ$]

$$\alpha = \frac{\Delta R}{R_0 \Delta t} = \frac{116 \Omega - 100 \Omega}{(100 \Omega)(40 \text{ C}^\circ)}; \quad \alpha = 0.00400 / \text{C}^\circ$$

27-26. A length of copper ($\alpha = 0.0043/\text{C}^\circ$) wire has a resistance of 8Ω at 20°C . What is the resistance at 90°C ? At -30°C ?

$$\Delta R = (0.0043/\text{C}^\circ)(8 \Omega)(70 \text{ C}^\circ) = 2.41 \Omega; \quad R = 8.00 \Omega + 2.41 \Omega = 10.41 \Omega$$

$$\Delta R = (0.0043/\text{C}^\circ)(8 \Omega)(-30^\circ\text{C} - 20^\circ\text{C}) = -1.72 \Omega; \quad R = 8.00 \Omega - 1.72 \Omega = 6.28 \Omega$$

*27-27. The copper windings ($\alpha = 0.0043/\text{C}^\circ$) of a motor experience a 20 percent increase in resistance over their value at 20°C . What is the operating temperature?

$$\frac{\Delta R}{R} = 0.2; \quad \Delta t = \frac{\Delta R}{R_0 \alpha} = \frac{0.2}{0.0043/\text{C}^\circ} = 46.5 \text{ C}^\circ; \quad t = 20^\circ\text{C} + 46.5 \text{ C}^\circ = 66.5 \text{ C}^\circ$$

*27-28. The resistivity of copper at 20°C is $1.78 \times 10^{-8} \Omega \text{ m}$. What change in temperature will produce a 25 percent increase in resistivity?

Challenge Problems

27-29. A water turbine delivers 2000 kW to an electric generator which is 80 percent efficient and has an output terminal voltage of 1200 V. What current is delivered and what is the electrical resistance? [$P_{\text{out}} = (0.80)(2000 \text{ kW}) = 1600 \text{ kW}$]

$$P = VI; \quad I = \frac{P}{V} = \frac{1600 \times 10^3 \text{ W}}{1200 \text{ V}}; \quad I = 1330 \text{ A}$$

$$R = \frac{V}{I} = \frac{1200 \text{ V}}{1300 \text{ A}}; \quad R = 0.900 \Omega$$

27-30. A 110-V radiant heater draws a current of 6.0 A. How much heat energy in joules is delivered in one hour?

$$P = \frac{E}{t} = VI; \quad E = VI t = (110 \text{ V})(6 \text{ A})(3600 \text{ s}); \quad \boxed{E = 2.38 \text{ MJ}}$$

27-31. A power line has a total resistance of 4 k Ω . What is the power loss through the wire if the current is reduced to 6.0 mA?

$$P = I^2 R = (0.006 \text{ A})^2 (4000 \text{ } \Omega); \quad \boxed{P = 144 \text{ mW}}$$

27-32. A certain wire has a resistivity of $2 \times 10^{-8} \text{ } \Omega \cdot \text{m}$ at 20°C . If its length is 200 m and its cross section is 4 mm^2 , what will be its electrical resistance at 100°C . Assume that $\alpha = 0.005/\text{C}^\circ$ for this material. [$\Delta t = 100^\circ\text{C} - 20^\circ\text{C} = 80 \text{ C}^\circ$]

$$R_0 = \frac{\rho l}{A} = \frac{(2 \times 10^{-8} \text{ } \Omega \cdot \text{m})(200 \text{ m})}{4 \times 10^{-6} \text{ m}^2}; \quad R_0 = 1.00 \text{ } \Omega \quad \text{at } 20^\circ\text{C}$$

$$R = R_0 + \alpha R_0 \Delta t = 1.00 \text{ } \Omega + (0.005/\text{C}^\circ)(1 \text{ } \Omega)(80 \text{ C}^\circ); \quad \boxed{R = 1.40 \text{ } \Omega}$$

27-33. Determine the resistivity of a wire made of an unknown alloy if its diameter is 0.007 in. and 100 ft of the wire is found to have a resistance of 4.0 Ω . [$D = 0.007 \text{ in.} = 7 \text{ mil}$]

$$A = (7 \text{ mil})^2 = 49 \text{ cmil}; \quad R = \frac{\rho l}{A}; \quad \rho = \frac{RA}{l}$$

$$\Delta = \frac{RA}{l} = \frac{(4 \text{ } \Omega)(49 \text{ cmil})}{100 \text{ ft}}; \quad \boxed{\rho = 1.96 \text{ } \Omega \text{ cmil/ft}}$$

27-34. The resistivity of a certain wire is $1.72 \times 10^{-8} \text{ } \Omega \cdot \text{m}$ at 20°C . A 6-V battery is connected to a 20-m coil of this wire having a diameter of 0.8 mm. What is the current in the wire?

$$A = \frac{\pi D^2}{4} = \frac{\pi(0.0008 \text{ m})^2}{4} = 5.03 \times 10^{-7} \text{ m}^2; \quad R = \frac{\rho l}{A}$$

$$27-34. \text{ (Cont.)} \quad R = \frac{\rho l}{A} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(20 \text{ m})}{5.03 \times 10^{-7} \text{ m}^2}; \quad R = 0.684 \Omega$$

$$I = \frac{V}{R} = \frac{6.00 \text{ V}}{0.684 \Omega}; \quad \boxed{I = 8.77 \text{ A}}$$

27-35. A certain resistor is used as a thermometer. Its resistance at 20⁰C is 26.00 Ω , and its resistance at 40⁰C is 26.20 Ω . What is the temperature coefficient of resistance for this material?

$$\alpha = \frac{\Delta R}{R_0 \Delta t} = \frac{(26.20 \Omega - 26.00 \Omega)}{(26.00 \Omega)(40^{\circ}\text{C} - 20^{\circ}\text{C})}; \quad \boxed{\alpha = 3.85 \times 10^{-4}/\text{C}^{\circ}}$$

*27-36. What length of copper wire at 20⁰C has the same resistance as 200 m of iron wire at 20⁰C? Assume the same cross section for each wire. [*Product RA doesn't change.*]

$$R = \frac{\rho l}{A}; \quad RA = \rho l; \quad \rho_1 R_1 = \rho_2 l_2; \quad l_2 = \frac{\rho_1 l_1}{\rho_2}$$

$$l_2 = \frac{\rho_1 l_1}{\rho_2} = \frac{(9.5 \times 10^{-8} \Omega \cdot \text{m})(200 \text{ m})}{1.72 \times 10^{-8} \Omega \cdot \text{m}}; \quad \boxed{l_2 = 1100 \text{ m}}$$

*27-37. The power loss in a certain wire at 20⁰C is 400 W. If $\alpha = 0.0036/\text{C}^{\circ}$, by what percentage will the power loss increase when the operating temperature is 68⁰C?

$$\Delta R = \alpha R_0 \Delta t; \quad \frac{\Delta R}{R} = (0.0036/\text{C}^{\circ})(68^{\circ}\text{C} - 20^{\circ}\text{C}) = 0.173$$

Since $P = I^2 R$, the power loss increases by same percentage: $\boxed{17.3 \%}$

Critical Thinking Problems

27-38. A 150- Ω resistor at 20⁰C is rated at 2.0 W maximum power. What is the maximum voltage that can be applied across the resistor with exceeding the maximum allowable power? What is the current at this voltage?

$$P = \frac{V^2}{R}; \quad V = \sqrt{PR} = \sqrt{(2.00 \text{ W})(150 \Omega)}; \quad \boxed{V = 17.3 \text{ V}}$$

27-39. The current in a home is alternating current, but the same formulas apply. Suppose a fan motor operating a home cooling system is rated at 10 A for a 120-V line. How much energy is required to operate the fan for a 24-h period? At a cost of 9 cents per kilowatt-hour, what is the cost of operating this fan continuously for 30 days?

$$P = VI = (110 \text{ V})(10 \text{ A}) = 1100 \text{ W}; \quad E = Pt = (1100 \text{ W})(24 \text{ h}) = 26.4 \text{ kW h}$$

$$E = (26.4 \text{ kW h})(3600 \text{ s/h})(1000 \text{ W/kW}); \quad \boxed{E = 95.0 \text{ MJ}}$$

$$\text{Cost} = 26.4 \frac{\text{kW} \cdot \text{h}}{\text{day}} \left(\frac{\$0.08}{\text{kW} \cdot \text{h}} \right) (30 \text{ days}); \quad \boxed{\text{Cost} = \$53.36}$$

*27-40. The power consumed in an electrical wire ($\alpha = 0.004/\text{C}^0$) is 40 W at 20⁰C. If all other factors are held constant, what is the power consumption when (a) the length is doubled, (b) the diameter is doubled, (c) the resistivity is doubled, and (d) the absolute temperature is doubled? (*Power loss is proportional to resistance R*)

$$R = \frac{\rho l}{A}; \quad P \propto l; \quad P \propto \frac{1}{A}; \quad P \propto \Delta R \propto \Delta T$$

(a) *Double length and double power loss:* $\text{Loss} = 2(40 \text{ W}) = \boxed{80 \text{ W}}$

(b) *doubling diameter gives $4A_0$ and one-fourth power loss:* $\text{Loss} = \frac{1}{4}(40 \text{ W}) = \boxed{10 \text{ W}}$

(c) *Doubling resistivity doubles resistance, and also doubles power loss:* $\text{Loss} = \boxed{80 \text{ W}}$

*27-40. (Cont.) (d) $T = (20^0 + 273^0) = 293 \text{ K}$; $\Delta T = 2T - T = T$; $\Delta T = 293 \text{ K} = 293 \text{ C}^0$

If absolute temperature doubles, the new resistance is given by:

$$R = R_0(1 + \alpha\Delta T); \quad \frac{R}{R_0} = 1 + (0.004/\text{C}^0)(293 \text{ C}^0) = 2.172;$$

$$\frac{P}{P_0} = \frac{R}{R_0} = 2.172; \quad \text{Loss} = 2.172(40 \text{ W}); \quad \boxed{\text{Loss} = 86.9 \text{ W}}$$

This of course presumes that resistivity remains linear, which is not likely.

*27-41. What must be the diameter of an aluminum wire if it is to have the same resistance as an equal length of copper wire of diameter 2.0 mm? What length of nichrome wire is needed to have the same resistance as 2 m of iron wire of the same cross section?

$$R = \frac{\rho l}{A}; \quad \frac{R}{l} = \frac{\rho}{A} = \text{const.}; \quad \frac{\rho_c}{A_c} = \frac{\rho_a}{A_a}; \quad A = \frac{\pi D^2}{4}; \quad \frac{\rho_c}{(D_c)^2} = \frac{\rho_a}{(D_a)^2}$$

$$D_a^2 = \frac{\rho_a D_c^2}{\rho_c}; \quad D_a = D_c \sqrt{\frac{\rho_c}{\rho_a}} = (2 \text{ mm}) \sqrt{\frac{1.72 \times 10^{-8} \Omega \cdot \text{m}}{2.80 \times 10^{-8} \Omega \cdot \text{m}}}; \quad \boxed{D_a = 1.57 \text{ mm}}$$

$$R = \frac{\rho l}{A}; \quad RA = \rho l = \text{const.}; \quad \rho_n l_n = \rho_i l_i; \quad l_n = \frac{\rho_i l_i}{\rho_n}$$

$$l_n = \frac{\rho_i l_i}{\rho_n} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})}{(100 \times 10^{-8} \Omega \cdot \text{m})}; \quad \boxed{l_n = 1.72 \text{ cm}}$$

*27-42. An iron wire ($\alpha = 0.0065/\text{C}^0$) has a resistance of 6.00Ω at 20^0C and a copper wire ($\alpha = 0.0043/\text{C}^0$) has a resistance of 5.40Ω at 20^0C . At what temperature will the two wires have the same resistance? [Conditions: $\alpha_i R_{oi} \Delta t_i - \alpha_c R_{oc} \Delta t_c = 6 \Omega - 5.4 \Omega = -0.60 \Omega$.]

$$\Delta t = \frac{-0.600 \Omega}{\alpha_i R_{oi} - \alpha_c R_{oc}} = \frac{-0.600 \Omega}{(0.0065/\text{C}^0)(6.0 \Omega) - (0.0043/\text{C}^0)(5.4 \Omega)}; \quad \Delta t = -38.0 \text{ C}^0$$

$$\Delta t = t_f - 20^0 = -38.0 \text{ C}^0; \quad \boxed{t_f = -18.0^0\text{C}}$$

This document was created with Win2PDF available at <http://www.win2pdf.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.